

Body Composition (BC) Calculations

Variables:

- Excitation Frequency
- Excitation Voltage
- Unknown Impedance
- Access Impedance
- Calibration Resistor (R_{CAL})
- TIA Resistor (R_{TIA})
- Instrumentation Amplifier Gain Resistor (R_G)

Excitation Frequency:

High frequency excitation is required for BC measurements. Good accuracy is achieved using 50 kHz.

Excitation Voltage:

Large excitation voltage used to achieve best SNR. 600 mV_{PEAK} recommended.

Unknown Impedance:

The impedance range of unknown impedance ($Z_{UNKNOWN}$) for BC applications (4 electrode, wrist worn BC solution) is typically 100 Ω - 5 k Ω (from left wrist to right finger).

Access Impedance:

Current limiting resistor (R_{LIMIT}) and DC blocking / isolating capacitors (C_{ISO1} and C_{ISO2}) are required to meet the IEC 60601 Standard. These components will contribute towards the total access impedance of the excitation leg ($Z_{ACCESS1}$) and measurement leg ($Z_{ACCESS2}$).

$$Z_{ACCESS1} = R_{LIMIT} + C_{ISO1}$$

$$Z_{ACCESS2} = C_{ISO2}$$

R_{LIMIT} :

IEC 60601 Standard limit for patient leakage at 50 kHz is 500 μA_{RMS}

$$500 \mu A_{RMS} = 707 \mu A_{PEAK}$$

$$600 \text{ mV}_{PEAK} / 707 \mu A_{PEAK} = 848 \Omega$$

Use 1 k Ω for additional safety margin.

C_{ISO} :

C_{ISO} should be large, but also needs to be cost effective. 47 nF should satisfy both metrics.

Calibration Resistor (R_{CAL}):

R_{CAL} should be set to be close to the minimum value of the expected unknown impedance. In this example, close to 100 Ω

TIA Resistor (R_{TIA}):

For R_{TIA} calculations use the minimum $Z_{UNKNOWN}$.

$$\text{Minimum impedance seen by the TIA} = Z_{ACCESS1} + Z_{UNKNOWN} + Z_{ACCESS2} = 1108.31 \Omega - 7.02^\circ$$

$$600 \text{ mV}_{PEAK} / 1108.31 \Omega = 541 \mu A_{PEAK}$$

$$\text{Max ADC range} = 750 \text{ mV}_{PEAK}$$

To avoid non-linearities at the ends of the range, use 80% of the total range = 600 mV

$$600 \text{ mV}_{PEAK} / 541 \mu A = 1108 \Omega$$

Use $R_{TIA} = 1 \text{ k}\Omega$

Instrumentation Amplifier (AD8226) Gain Resistor (R_G):

Maximum impedance of Z_{UNKNOWN} = 5 kΩ

Maximum current into TIA = 541 μA

Maximum voltage drop across R_{TIA} = 1 kΩ * 541 μA = 541 mV

ADuCM350 max ADC range = 750 mV_{PEAK}

Gain required = 750 mV / 541 mV = 1.386

AD8226 gain G = 1 + (49.4 kΩ / R_G) = 1.386 (see AD8226 datasheet for details)

R_G = 127.98 kΩ

Use R_G = 120 kΩ

Note if 2-Wire Relative Measurement Only:

Same maths apply for ADuCM350 – ignore AD8226 maths – part is not required.

RCAL measurement will need to be included so use the 2-Wire Impedance measurement example in SDK.