

$$R10=32 / IDRAIN (90 \text{ mA}) = 355 \text{ Ohm}$$

$$VDD=VDRAIN (4V) + IDRAIN (90 \text{ mA}) \times RDS\_ON (5 \text{ Ohm}) = 4.45V$$

