

$$R10 = 150 / I_{DRAIN} (2.4A) = 62.5 \text{ Ohm}$$

$$V_{DD} = V_{DRAIN} + I_{DRAIN} (1.2A) \times R_{DS_ON} (0.85\text{Ohm})$$

