

*Circuits from the Lab™ tested circuit designs address common design challenges and are engineered for quick and easy system integration. For more information and/or support, visit [www.analog.com/CN0179](http://www.analog.com/CN0179).*

Devices Connected/Referenced	
AD8657	18V, Precision, Micropower CMOS Rail-to-Rail I/O Dual Operational Amplifier
ADR125	Precision, Micropower LDO Voltage Reference in TSOT
AD5621	2.7 V to 5.5 V, <100 $\mu$ A, 12-Bit nanoDAC, SPI Interface

## Less Than 200 $\mu$ A, Low Power, 4 mA-to-20 mA, Process Control Current Loop

### CIRCUIT FUNCTION AND BENEFITS

The circuit in Figure 1 is a 4 mA-to-20 mA current loop transmitter for communication between a process control system and its actuator. Besides being cost effective, this circuit offers the industry's lowest power solution. The 4 mA-to-20 mA current loop has been used extensively in programmable logic controllers (PLCs) and distributed control systems (DCS's), with digital or analog inputs and outputs. Current loop interfaces are usually preferred because they offer the most cost effective approach to long distance noise immune data transmission. The combination of the low power AD8657 dual op amp, AD5621 DAC, and ADR125 reference allows more power budget for higher power devices, such as microcontrollers

and digital isolators. The circuit output is 0 mA to 20 mA of current. The 4 mA to 20 mA range is usually mapped to represent the input control range from the DAC or microcontroller, while the output current range of 0 mA to 4 mA is often used to diagnose fault conditions.

The 12-bit, 5 V AD5621 requires 75  $\mu$ A typical supply current. The AD8657 is a rail-to-rail input/output dual op amp and is one of the lowest power amplifiers currently available in the industry (22  $\mu$ A over the full supply voltage and input common-mode range) with high operating voltage of up to 18 V. The ADR125 precision micropower 5 V band gap reference requires only 95  $\mu$ A. Together, these three devices consume a typical supply current of 192  $\mu$ A.

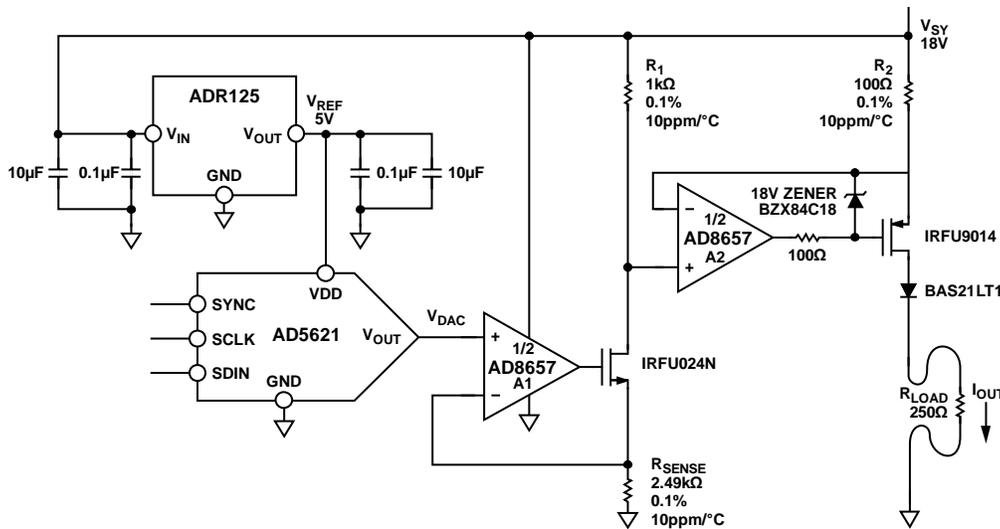


Figure 1. Low Power 4 mA-to-20 mA Process Control Current Loop (Simplified Schematic: All Connections and Decoupling Not Shown)

### Rev. 0

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

## CIRCUIT DESCRIPTION

For industrial and process control modules, 4 mA-to-20 mA current loop transmitters are used as a means of communication between the control unit and the actuator. Located at the control unit, the 12-bit [AD5621](#) DAC produces an output voltage,  $V_{DAC}$ , between 0 V and 5 V as a function of the input code. The code is set via an SPI interface. The ideal relationship between the input code and output voltage is given by

$$V_{DAC} = V_{REF} \times (D/2^{12}) \quad (1)$$

where:

$V_{REF}$  is the output of [ADR125](#) and the power supply to the [AD5621](#).

$D$  is the decimal equivalent of the binary code that is loaded to the [AD5621](#).

The DAC output voltage sets the current flowing through the sense resistor,  $R_{SENSE}$ , where

$$I_{SENSE} = V_{DAC}/R_{SENSE} \quad (2)$$

The current through  $R_{SENSE}$  varies from 0 mA to 2 mA as a function of  $V_{DAC}$ . This current develops a voltage across  $R1$  and sets the voltage at the noninverting input of the [AD8657](#) amplifier (A2). The A2 [AD8657](#) closes the loop and brings the inverting input voltage to the same voltage as the noninverting input. Therefore, the current flowing through  $R1$  is mirrored by a factor of 10 to  $R2$ . This is represented by Equation 3.

$$I_{OUT} = I_{R2} = (V_{DAC}/R_{SENSE}) \times (R1/R2) \quad (3)$$

With  $V_{DAC}$  ranging from 0 V to 5 V, the circuit generates a current output from 0 mA to 20 mA.

The [AD5621](#) is a 12-bit DAC from the *nanoDAC* family and operates from the 5 V output voltage of the [ADR125](#) reference. It has an on-chip precision output buffer that is capable of swinging from rail-to-rail, thus allowing a high dynamic output range. With a supply voltage of 5 V, [AD5621](#) consumes a typical 75  $\mu$ A of supply current.

In addition, this circuit solution requires a rail-to-rail input amplifier. The [AD8657](#) dual op amp is an excellent choice, with low power and rail-to-rail features. The op amp operates with a typical supply current of 22  $\mu$ A over the specified supply voltage and input common-mode voltage. It also offers excellent noise and bandwidth per unit of current. The [AD8657](#) is one of the lowest power amplifiers that operates on supplies of up to 18 V.

The [ADR125](#) is a precision, micropower, low dropout (LDO) voltage reference. With an 18 V input voltage, quiescent current is only 95  $\mu$ A, typical. An LDO voltage reference is preferred because more voltage drop can be tolerated across the loop wires from the control unit to the actuators. The [ADR125](#) requires a small 0.1  $\mu$ F capacitor at its output for stability. An additional 0.1  $\mu$ F to 10  $\mu$ F capacitor in parallel can improve load transient response. Input capacitors, though not required, are recommended. A 1  $\mu$ F to 10  $\mu$ F capacitor on the input improves transient response if there is a sudden supply voltage change. An additional 0.1  $\mu$ F capacitor in parallel also helps reduce noise from the supply.

Bypass capacitors (not shown in Figure 1) are required. In this case, a 10  $\mu$ F tantalum capacitor in parallel with a 0.1  $\mu$ F ceramic capacitor should be placed on each power pin of each dual op amp. Details of proper decoupling techniques can be found in [Tutorial MT-101](#).

The circuit solution outputs 0 mA to 20 mA of current. Figure 2 shows the measured output current from the circuit into the 250  $\Omega$  load resistor. Figure 3 shows the output current error plot.

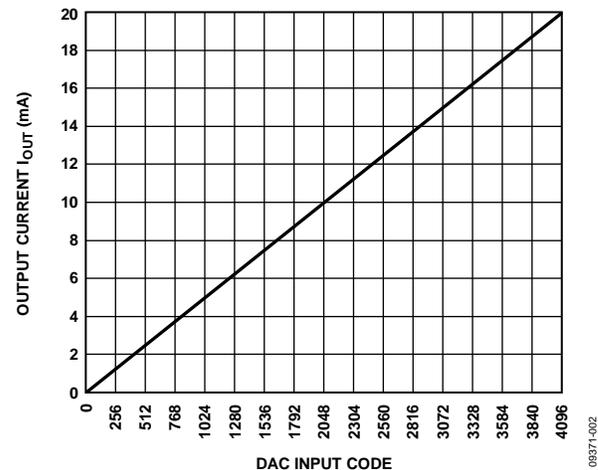


Figure 2. 0 mA to 20 mA Output Current

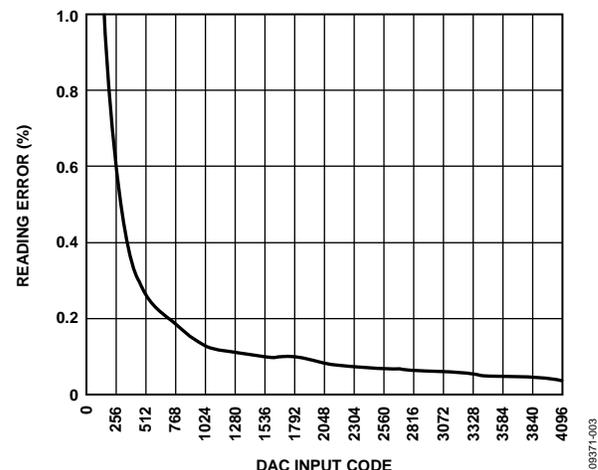


Figure 3. Output Current Error Plot

## COMMON VARIATIONS

For a 14-bit or 16-bit resolution solution, consider the [AD5641](#) or [AD5662](#), respectively. The 16 V CMOS [ADA4665-2](#) op amp is another option to replace the AD8657. It is more cost effective and has lower voltage noise at the expense of a higher supply current.

When selecting amplifiers for this application, always make sure that the input common-mode voltage range and the supply voltage are not exceeded.

For a higher supply voltages, consider the [ADR02](#) voltage reference, which can operate on supply voltages of up to 36 V.

## LEARN MORE

[AN-202 Application Note, An IC Amplifier User's Guide to Decoupling, Grounding, and Making Things Go Right for a Change](#), Analog Devices.

[AN-345 Application Note, Grounding for Low- and High-Frequency Circuits](#), Analog Devices.

[AN-347 Application Note, Shielding and Guarding: How to Exclude Interference-Type Noise](#), Analog Devices.

Colm Slattery, Derrick Hartmann, and Li Ke, "PLC Evaluation Board Simplifies Design of Industrial Process Control Systems," *Analog Dialogue* (April 2009).

Jung, Walt. *Op Amp Applications*, Analog Devices. Also available as *Op Amp Applications Handbook*, Elsevier.

Kester, Walt. 2005. *The Data Conversion Handbook*. Chapters 3 and 7. Analog Devices.

MT-015 Tutorial, *Basic DAC Architectures II: Binary DACs*. Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*. Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*. Analog Devices. Voltage Reference Wizard Design Tool.

## Data Sheets

[AD8657 Data Sheet](#)

[ADR125 Data Sheet](#)

[AD5621 Data Sheet](#)

[AD5641 Data Sheet](#)

[AD5662 Data Sheet](#)

[ADA4665-2 Data Sheet](#)

[ADR02 Data Sheet](#)

## REVISION HISTORY

12/10—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, "Circuits from the Lab" are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

©2010 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.  
CN09371-0-12/10(0)



www.analog.com