

$$i1 = i_{b-} + i2 \dots \textcircled{1}$$

$$i2 = i_{b+} + i4 \dots \textcircled{2}$$

$$i1 = \frac{V1 - Va}{R1}$$

$$i2 = \frac{Va - Vout}{R2}$$

$$i3 = \frac{V2 - Vb}{R3}$$

$$i4 = \frac{Vb}{R4}$$

From  $\textcircled{1}$   $\frac{V1 - Va}{R1} = i_{b-} + \frac{Va - Vout}{R2}$

$$\frac{V1}{R1} + \frac{Vout}{R2} - i_{b-} = \frac{Va}{R2} + \frac{Va}{R1}$$

$$Va = \left[ \frac{V1}{R1} + \frac{Vout}{R2} - i_{b-} \right] \left[ \frac{1}{\frac{1}{R1} + \frac{1}{R2}} \right] \dots \textcircled{3}$$

From ②  $\frac{V2 - Vb}{R3} = ib+ + \frac{Vb}{R4}$    $\frac{V2}{R3} + Ib+ = Vb \left( \frac{1}{R3} + \frac{1}{R4} \right)$


$$Vb = \left( \frac{V2}{R3} - ib+ \right) \left( \frac{1}{\frac{1}{R3} + \frac{1}{R4}} \right) \dots \textcircled{4}$$

OPA  
formula

$$Vout = A (Vb - Va + Voffset) \quad \text{Insert } \textcircled{3} \textcircled{4}$$

$$Vout = A \left( \left( \frac{V2}{R3} - ib+ \right) \left( \frac{R3 R4}{R3 + R4} \right) - \left( \frac{V1}{R1} + \frac{Vout}{R2} - ib- \right) \left( \frac{R1 R2}{R1 + R2} \right) + Voffset \right)$$

$$Vout + A \frac{Vout R1}{R1 + R2} = A \left( \left( \frac{V2}{R3} - ib+ \right) \left( \frac{R3 R4}{R3 + R4} \right) - \left( \frac{V1}{R1} - ib- \right) \left( \frac{R1 R2}{R1 + R2} \right) + Voffset \right)$$



$$Vout \left( 1 + \frac{R1}{R1 + R2} A \right) =$$

$$V_{out} = \frac{\frac{R_4}{R_3 + R_4} V_2 - \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1 R_2}{R_1 + R_2} i_{b-} - \frac{R_3 R_4}{R_3 + R_4} + V_{offset}}{\frac{1}{A} + \frac{R_1}{R_1 + R_2}}$$

$$A \rightarrow \infty$$

$$V_{out} = \frac{R_4}{R_1} \frac{R_1 + R_2}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1 + R_2 i_{b-} - \frac{R_3 R_4}{R_1} \frac{R_1 + R_2}{R_3 + R_4} i_{b+} + \frac{R_1 + R_2}{R_1} V_{offset}$$

...⑤

$$\frac{R_2}{R_1} = \frac{R_4}{R_3} = 10$$

$$V_{out} = \frac{\frac{10}{1 + 10} V_2 - \frac{10}{1 + 10} V_1 + \frac{R_2}{1 + 10} i_{b-} - \frac{R_4}{1 + 10} i_{b+} + V_{offset}}{\frac{1}{A} + \frac{1}{1 + 10}}$$

$$\frac{1}{A} + \frac{1}{1 + 10}$$

$$V_{out} = 10(V_2 - V_1) + R_2 i_{b-} - R_4 i_{b+} + 11V_{offset}$$

In Datasheet Relation  $I_{os}$  &  $I_b$  @ Note 9

$$I_{os} \times 22.5k + I_b \times 22.5k \left(1 - \frac{R_p}{R_n}\right) \quad \rightarrow \quad 22.5k(I_{os} + I_b) - I_b 22.5k \frac{R_p}{R_n}$$

⑤  $i_{b+}$ ,  $i_{b-}$

$$V_{out} = \frac{R_4}{R_1} \frac{R_1 + R_2}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1 + R_2 i_{b-} - \frac{R_3 R_4}{R_1} \frac{R_1 + R_2}{R_3 + R_4} i_{b+} + \frac{R_1 + R_2}{R_1} V_{offset} \dots \textcircled{5}$$

$$R_p = R_3 + R_4 ??$$

$$R_n = R_1 + R_2 ??$$