

Condition


AD6674  $V_{com} = 2.05V$   $V_{NPP} = 1.7V$

Single End


$R_{IN} = 91.7\Omega$

ADL5569  $V_{com} \approx 2.5V$

$R_G = 500\Omega$   $R_F = 500\Omega$

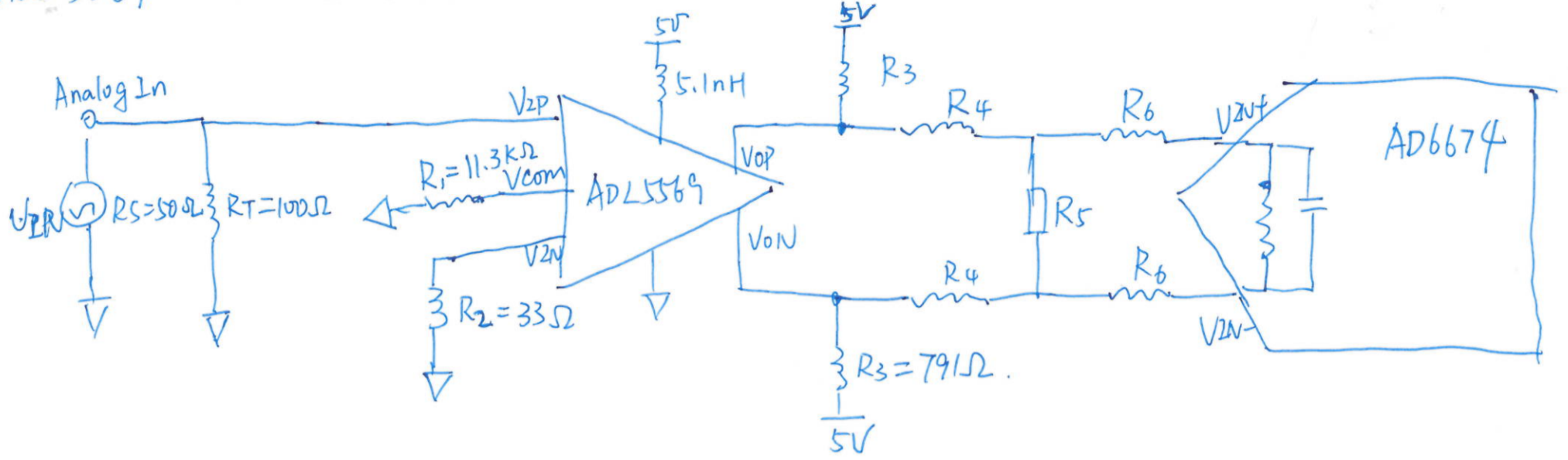

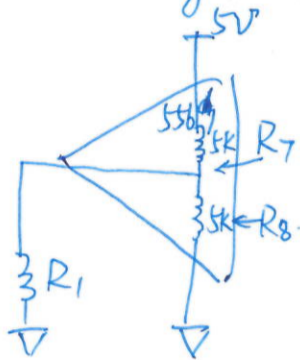Step 1.  $R_1$  for  $V_{com}$  setting to  $2.05V$




$$R_x = R_1 \parallel R_8$$

$$\frac{R_x}{R_x + R_7} = \frac{2.05}{5} \quad R_x = 3.47k\Omega$$

$$\therefore R_1 = 11.34k\Omega$$

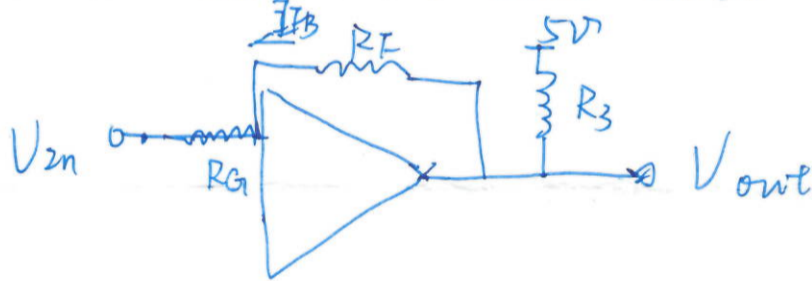Step 2. Assume  $V_{LO} = 0V$ ,  $V_{out} = 2.05V$




$$I_{FB} = \frac{V_{out} - V_{in}}{R_G + R_F} = \frac{2.05}{550} = 3.73mA$$

$$R_3 = \frac{V_{DD} - V_{com}}{I_{FB}} = \frac{5 - 2.05}{3.73mA} = 791\Omega$$

Step 3. As  $R_{IN}$  of ADL6674 is  $91.7\Omega$  per data sheet. To match  $50\Omega$   $R_S$

$$R_{IN} \parallel R_T = 50\Omega \quad \text{solve } R_T = 109.95$$

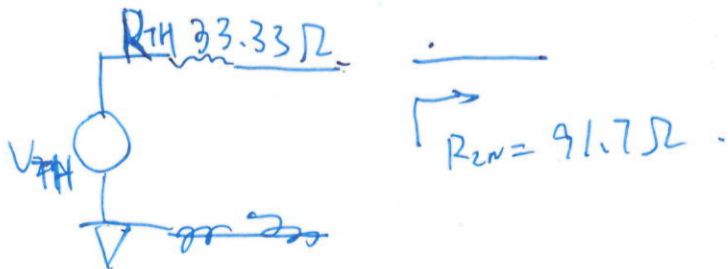make the  $R_T = 100\Omega$ . the Thevenin equivalent of Input is.



$V_{in}$  in series with a  $33.33\Omega$  Resistor -  
Connect  $R_2 = 33\Omega$  in  $V_{IN}$  to balance the two Input -

Step 4. Gain Adjustment

Assume the  $V_{out}$  desire =  $1.7V_{pp}$

$$\frac{1.7}{V_{TH}} = \frac{R_F}{R_G + R_{TH}}$$

Solve  $V_{TH} = 282mV_{pp}$

With Single to DIFF Attenuation of  $-3.5dB$

$$\frac{1.7}{V_{TH}} = \frac{500}{50 + 33}$$

$$\text{Gain} = 20 \log \left( \frac{500}{83} \right) = 15.6dB \quad 15.6 - 3.5 = 12.1dB$$

To get a  $1.7V_{pp}$  sig, the Input  $V_{in}$  should be  $0.43V_{pp}$